

Oscillators:


①

→ A circuit that converts a DC power source into a continuous, periodic alternating waveform at a specific frequency, without needing an external input signal.

→ Signal Generator.

→ Important for electrical and communication Engineering

Basic Structure:

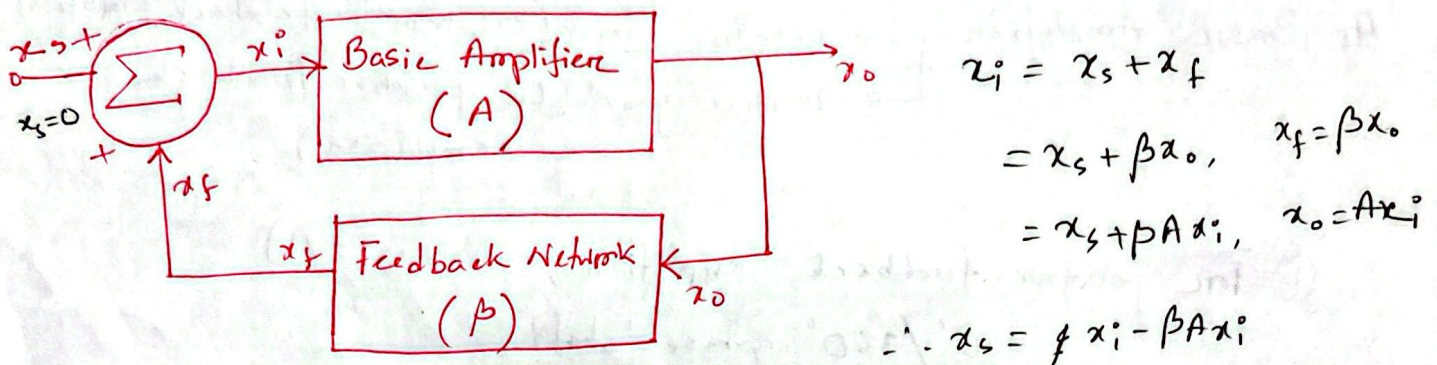

$$x_i = x_s + x_f$$

$$= x_s + \beta x_o, \quad x_f = \beta x_o$$

$$= x_s + \beta A x_i, \quad x_o = A x_i$$

$$\therefore x_s = x_i - \beta A x_i$$

$$= x_i (1 - \beta A)$$

signal flow diagram of Positive Feedback (FB) Amplifier.

* Oscillator circuits work on the principle of positive FB Amplifier.

Gain with feedback,

$$A_f = \frac{x_o}{x_s} = \frac{A x_i}{x_i (1 - \beta A)}$$

$$\therefore A_f = \frac{A}{1 - A\beta}, \quad A_f > A$$

If,

$$1 - A\beta = 0$$

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 - A\beta} = \infty$$

* It is possible to get an output signal x_o even with zero input signal, i.e., $x_s = 0$

$$\text{If } 1 - A\beta = 0 \Rightarrow A\beta = 1$$

$A\beta \rightarrow$ Loop Gain

$$x_f = \beta A x_i, \quad \text{Loop gain} = \frac{x_f}{x_i} = A\beta$$

$$x_f = x_i, \quad \text{if } A\beta = 1$$

Loop Gain (L) $A\beta = 1 \angle 0^\circ$

$$|L| = 1$$

$$\angle L = 0$$

Barkhausen Criterion
for sustained oscillation

* Feedback network $\Rightarrow$ Frequency Selective
Circuit (β)

Basic Amplifier $\begin{cases} \rightarrow \text{negative gain (CE, negative feedback amplifier)} \\ \rightarrow \text{positive gain (CB, positive feedback amplifier)} \end{cases}$

① For positive feedback amplifier, (Gain $+A$)
 $0^\circ/360^\circ$ phase shift.

Frequency Selective Circuit.
 $0^\circ/360^\circ$ phase shift.

② For negative feedback amplifier, (Gain $-A$)
 180° phase shift.

Frequency selective Circuit.
 180° phase shift.

Wein-Bridge Oscillator: (positive gain amplifier)

→ Basic Amp - Non-inverting amplifier (0° Phase shift)

→ FB Network → should provide 0° or 360° phase shift.

Loop Gain,

$$L = A\beta = 1 \angle 0^\circ$$

$$A = \frac{V_o}{V_f} = 1 + \frac{R_2}{R_1}$$

$$\beta = \frac{V_f}{V_o} = \frac{Z_p}{Z_p + Z_s}$$

$$L = \left(1 + \frac{R_2}{R_1}\right) \frac{Z_p}{Z_p + Z_s}$$

$$= \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + Z_s/Z_p}$$

$$= \frac{1 + R_2/R_1}{1 + Z_s/Z_p}$$


$$= \frac{1 + R_2/R_1}{1 + 1 + \frac{1}{j\omega R C} + j\omega R C + 1} = \frac{1 + R_2/R_1}{3 + \frac{1}{j\omega R C} + j\omega R C}$$

Loop gain, $L = A\beta$

$$= \frac{1 + R_2/R_1}{3 + \frac{1}{j\omega R C} + j\omega R C} = 1 \angle 0^\circ$$

$$\operatorname{Re}[L] = 1$$

$$\operatorname{Im}[L] = 0$$

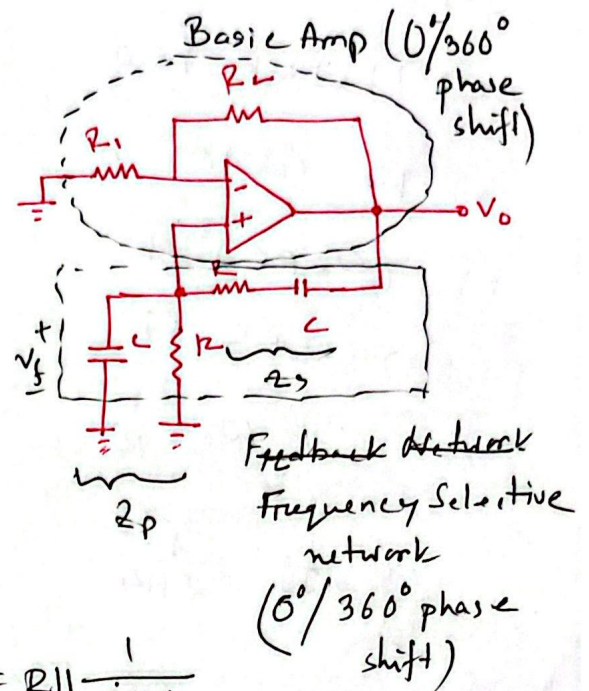

$$Z_p = R \parallel \frac{1}{j\omega C}$$

$$Z_s = R + \frac{1}{j\omega C}$$

$$\frac{1}{Z_p} = Y_p = \frac{1}{R} + j\omega C$$

$$\frac{1}{j\omega_0 RC} + j\omega_0 RC = 0$$

$$\Rightarrow 1 + (j\omega_0 RC)^2 = 0$$

$$\Rightarrow 1 - (\omega_0 RC)^2 = 0$$

$$\Rightarrow (\omega_0 RC)^2 = 1$$

$$\Rightarrow \omega_0 RC = 1$$

$$\therefore \omega_0 = \frac{1}{RC}$$

$$f_0 = \frac{1}{2\pi RC}$$

frequency of
oscillation

RC Phase Shift oscillator:

Negative Gain Amplifier.

Loop Gain,

$$L = A\beta = 1 \angle 0^\circ$$

$$\text{Re}[L] = 1$$

$$\text{Im}[L] = 0$$

Frequency of oscillation,

$$f_0 = \frac{1}{2\pi RC\sqrt{6}}$$

Gain of Basic Amp,

$$\frac{R_f}{R} = 29$$

$$\text{Re}[L] = 1$$

$$= \text{Re} \left[\frac{1 + R_2/R_1}{3 + \underbrace{1/j\omega RC + j\omega RC}_{=0}} \right] = 1$$

$$\text{Re}[L] = \frac{1 + R_2/R_1}{3} = 1$$

$$\Rightarrow 1 + R_2/R_1 = 3$$

$$\Rightarrow R_2/R_1 = 2$$

