

✓ Filters:

- ⇒ One of the most important circuit building blocks in electronic engineering.
- ⇒ Indispensable for communication systems and in most instrumentation systems.


Here,

- ① Try to understand the basic properties of 4 major filters.
- ② Learn the design and construction of filter circuits.
- ③ Drawing the bode plot

⇒ A two port network,

$V_i(s) \rightarrow$ input

$V_o(s) \rightarrow$ output.

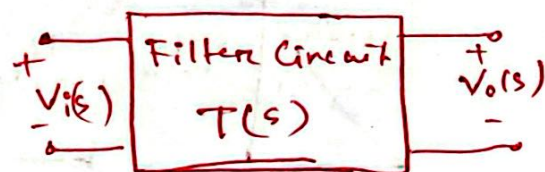


⇒ Ratio of V_o to V_i taken as a function of frequency is the Transfer function, $T(s)$

$$T(s) = \frac{V_o(s)}{V_i(s)} \quad s = j\omega \rightarrow \text{complex freq}^n$$


Types:

- Low pass filter → allows low freqⁿ signal to pass through.
- High Pass filter → allows high freqⁿ signal to pass through
- Band pass filter → allows a certain band of freqⁿ.
- Band stop filter → blocks signal within a certain band of freqⁿ.

Ideal Filter Characteristic -

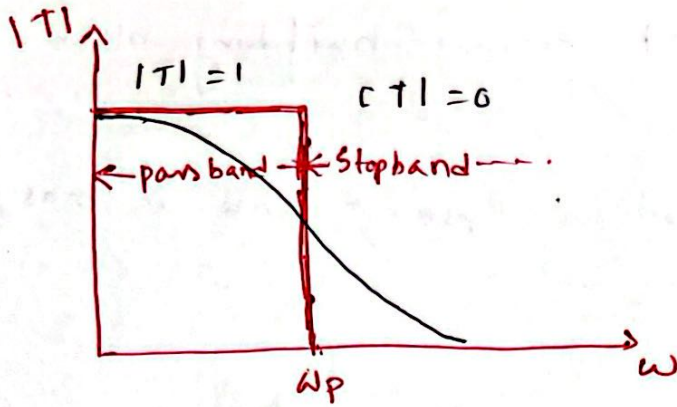


Low pass

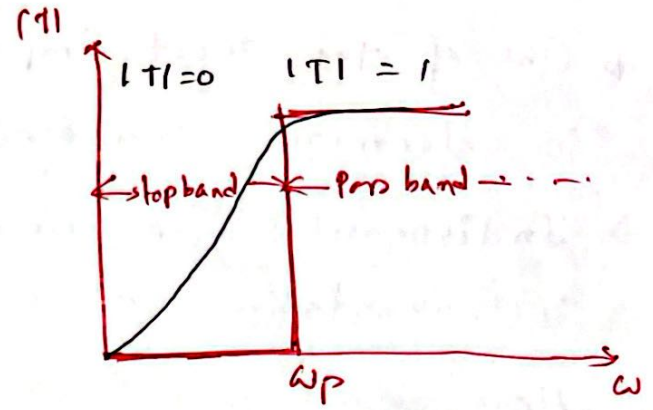


High pass

$\omega_p \rightarrow$ cut off freq

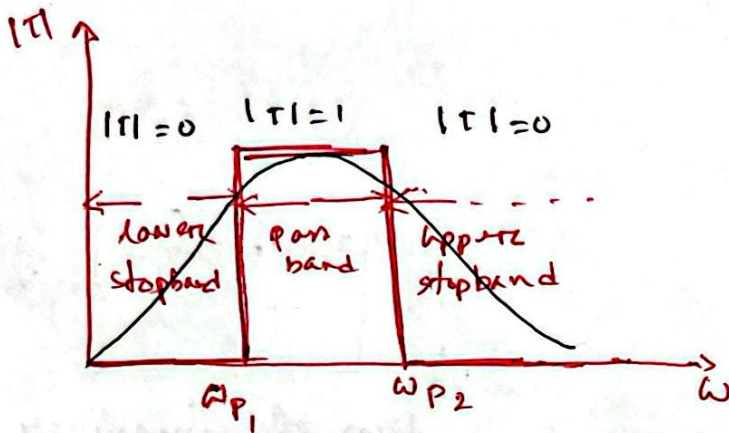

Band pass

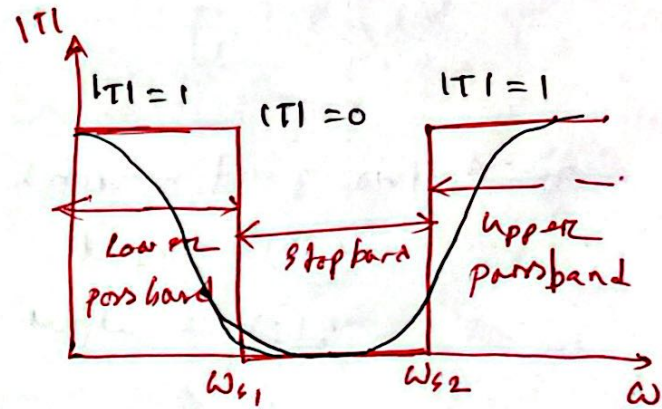


Band stop

$\omega_{p1}, \omega_{s1} \rightarrow$ lower cut off freq (ω_L)

$\omega_{p2}, \omega_{s2} \rightarrow$ higher cut off freq (ω_H)

Passive RC filters:


use passive electrical components.

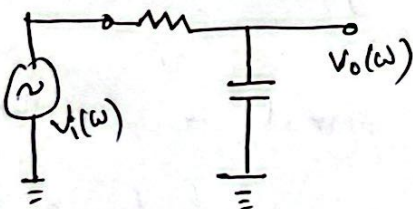

At $\omega = 0$



$$X_c = \frac{1}{\omega C} = \infty$$



$$T = \frac{V_o}{V_i} = 1$$

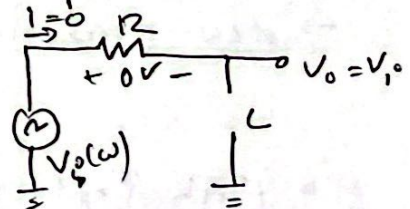

At $\omega = \infty$

$$X_c = \frac{1}{\omega C} = 0$$

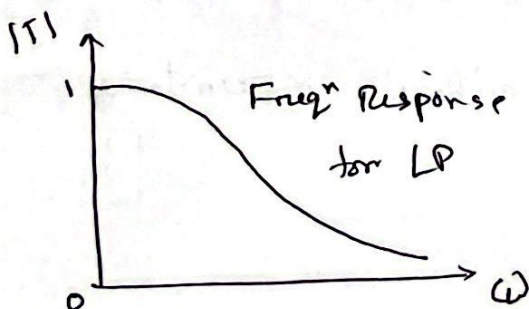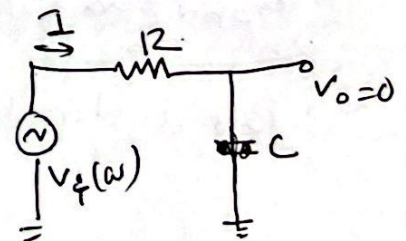

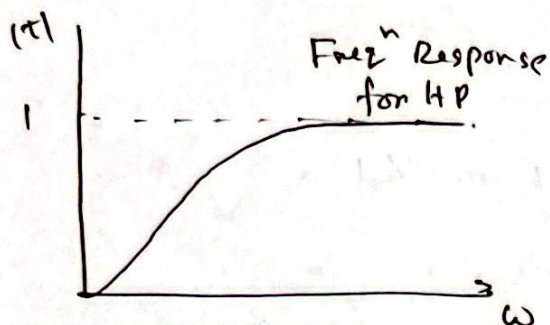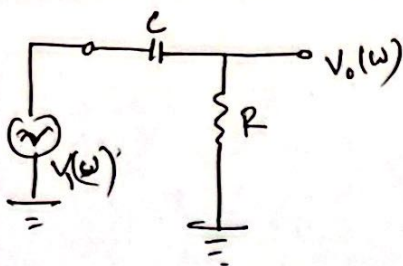

Transfer function:

$$\begin{aligned} \text{HP} \quad V_o &= \frac{R}{R + 1/j\omega C} V_i \\ &= \frac{1}{1 + 1/j\omega RC} V_i \end{aligned}$$

$$T(\omega) = \frac{V_o}{V_i} = \frac{1}{1 + 1/j\omega RC}$$


$$|T(\omega)| = \left| \frac{1}{1 + 1/j\omega RC} \right|$$

$$= \frac{1}{|1 + 1/j\omega RC|}$$

$$= \frac{1}{\sqrt{1 + (1/\omega RC)^2}} \quad \begin{aligned} &= 0, \omega = 0 \\ &= 1, \omega = \infty \end{aligned}$$

Cut off freqⁿ:

For low pass:

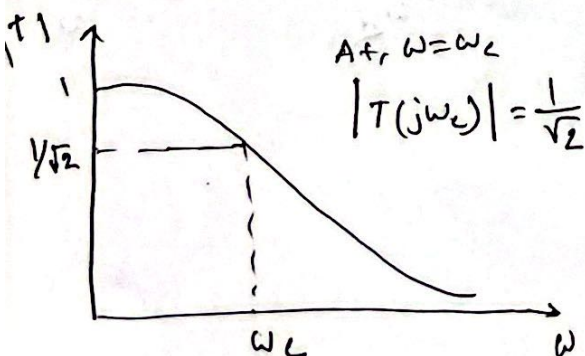

At, $\omega = 0$



$$X_C = \frac{1}{\omega C} = \infty$$

$$T = \frac{V_o}{V_i} = 0$$

At, $\omega = \infty$

$$X_C = \frac{1}{\omega C} = 0$$

$$T = \frac{V_o}{V_i} = 1$$

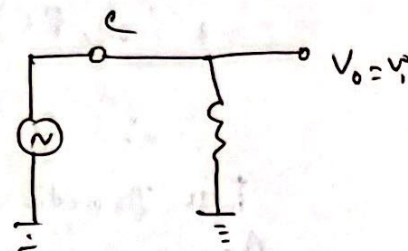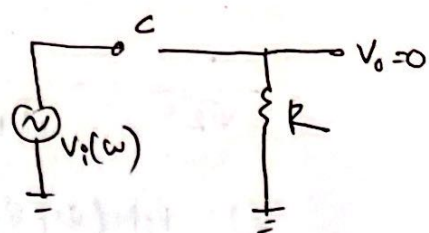

LP

$$V_o = \frac{1/j\omega C}{R + 1/j\omega C} V_i$$

$$= \frac{1}{1 + j\omega RC} V_i$$

$$\therefore T(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$\therefore |T(j\omega)| = \left| \frac{1}{1 + j\omega RC} \right|$$

$$= \frac{1}{|1 + j\omega RC|}$$

$$= \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \begin{aligned} &= 1, \omega = 0 \\ &= 0, \omega = \infty \end{aligned}$$

$$T(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega RC}$$

$$\therefore |T(j\omega)| = \frac{1}{|1 + j\omega RC|}$$

$$\therefore |T(j\omega_c)| = \frac{1}{|1 + j\omega_c RC|} = \frac{1}{\sqrt{2}}$$

$$\therefore \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (\omega_c RC)^2}}$$


$$\Rightarrow 1 + (\omega_c RC)^2 = 2$$

$$\Rightarrow (\omega_c RC)^2 = 1$$

$$\therefore \omega_c = \frac{1}{RC}$$

For practical use: gain can be > 1 or < 1 .
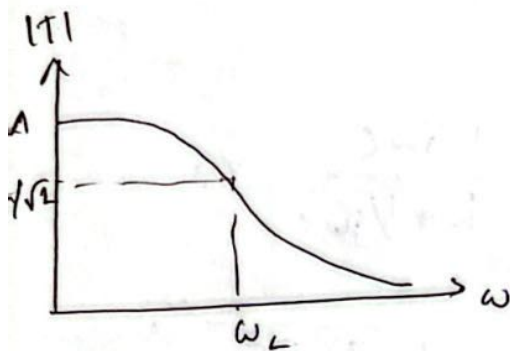
$$\text{Again, } T(j\omega) = \frac{V_o}{V_i}$$



$$= \frac{1}{1 + j\omega RC}$$

$$= \frac{1}{1 + j\omega/\omega_c} \quad [\omega_c = 1/RC]$$

$$\therefore T(s) = \frac{1}{1 + s/\omega_c}$$

$$T(s) = \frac{A_o}{1 + s/\omega_c}$$

$A_o = \text{max gain}$

General form of TF for LP

For HP:

$$T(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + 1/j\omega RC}$$


$$= \frac{1}{1 + \omega_c/j\omega}$$

$$\therefore T(s) = \frac{1}{1 + \omega_c/s} \quad s = j\omega$$

$$T(s) = \frac{A_o}{1 + \omega_c/s}$$

$A_o \rightarrow \text{max gain}$

General form of TF for HP

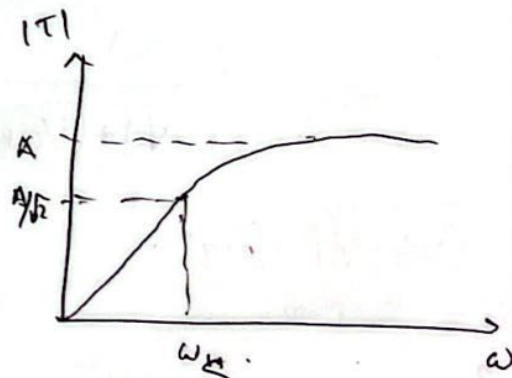

Passive RC filter with load:

$$Z_p = R_L \parallel \frac{1}{j\omega C}$$

$$V_o = \frac{Z_p}{R + Z_p} V_i = \frac{1}{1 + R/Z_p} V_i$$


$$T(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + R/Z_p}$$

$$= \frac{1}{1 + R\left(\frac{1}{R_L} + j\omega C\right)}$$

$$= \frac{1}{1 + \frac{R}{R_L} + \frac{R}{j\omega C} R j\omega C}$$

$$= \frac{1}{\frac{R+R_L}{R_L} + j\omega C R} \times \frac{R_L/(R+R_L)}{R_L/(R+R_L)}$$
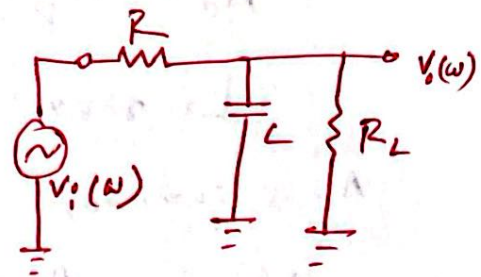
$$= \frac{R_L/(R+R_L)}{1 + j\omega C R R_L/(R+R_L)}$$



$\rightarrow R_L$ input resistor of the amplifier or microphone.

$$\frac{1}{Z_p} = Y_p = \text{Admittance} \\ = \frac{1}{R_L} + j\omega C$$

Now,

$$R_L/(R+R_L) = A_o = \text{constant}$$

$$R R_L/(R+R_L) = R \parallel R_L = R_p = \text{parallel equivalent}$$

$$\therefore T(j\omega) = \frac{V_o}{V_i} = \frac{A_o}{1 + j\omega C R_p}$$

$$\therefore T(s) = \frac{A_o}{1 + s C R_p} = \frac{A_o}{1 + \omega_{cl}/s}$$

$$\omega_{cl} = \frac{1}{C R_p} \gg \omega_c \quad (\omega_c = 1/RC)$$

$$R_p = R \parallel R_L < R$$

$\rightarrow$ Cut off freqⁿ with load

$$A_0 = \frac{R_L}{R + R_L} < 1$$

↳ max gain with load.

As a summary

$$\therefore T(s) = \frac{A_0}{1 + \omega_c s / \omega_c}$$

$$A_0 = \frac{R_L}{R + R_L} < 1$$


$$\omega_c = \frac{1}{R + R_L} > \omega_c$$

For RC Low pass without load

$$T(s) = \frac{1}{1 + \omega_c s / \omega_c}$$

$$\omega_c = \frac{1}{RC}$$


$$A_0 = 1$$

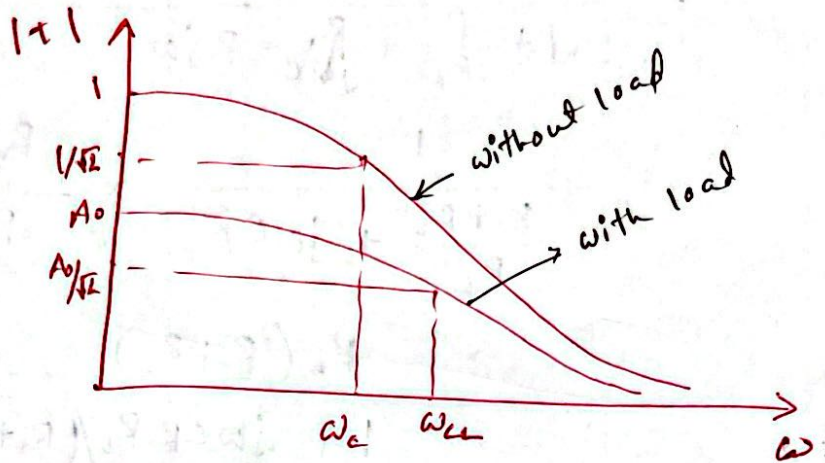

Drawback

changes filter characteristics }
 → unwanted signal introduction due to the increase in cut off freq
 → Lowers the gain of the system

Solⁿ

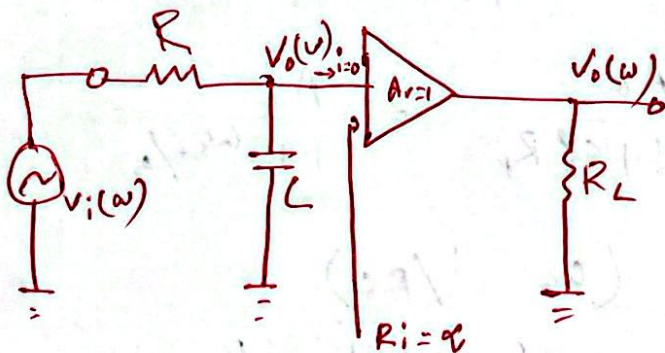

$$V_o = \frac{1/j\omega C}{R + 1/j\omega C} V_i$$

$$= \frac{1}{1 + j\omega CR} V_i$$


$$T(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega CR}$$

$$= \frac{1}{1 + j\omega/\omega_c}$$


$$T(s) = \frac{1}{1 + s/\omega_c}$$

Active LP:


2

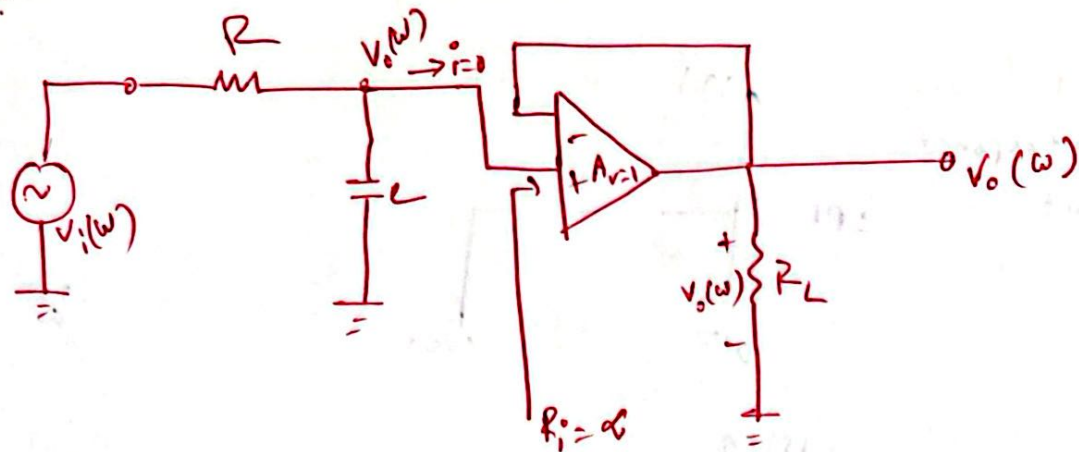


Active HP:

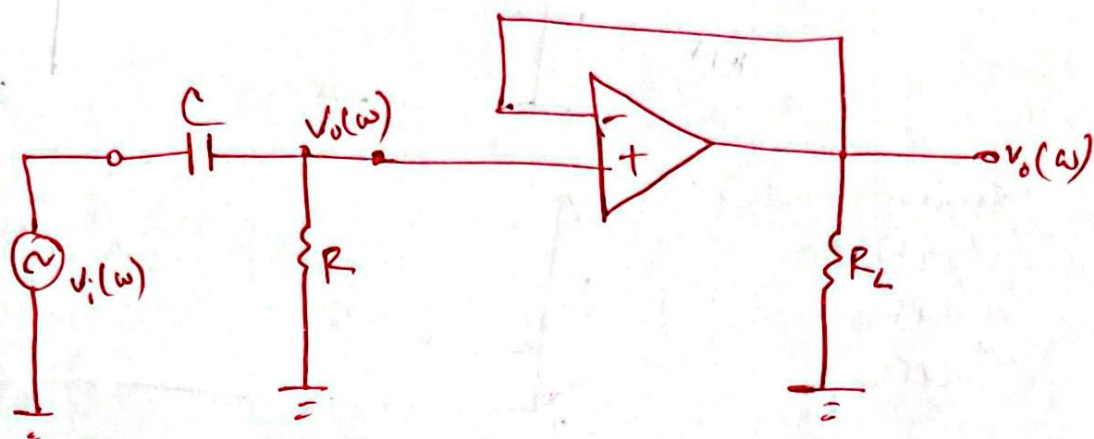

Bandpass and Bandstop filters:

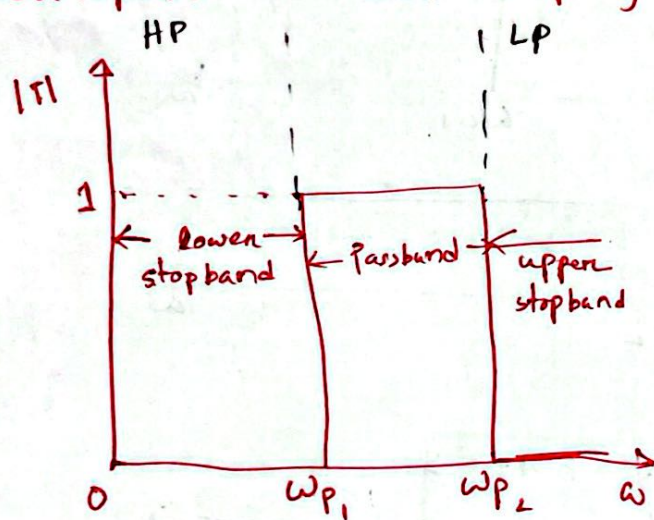


BPF

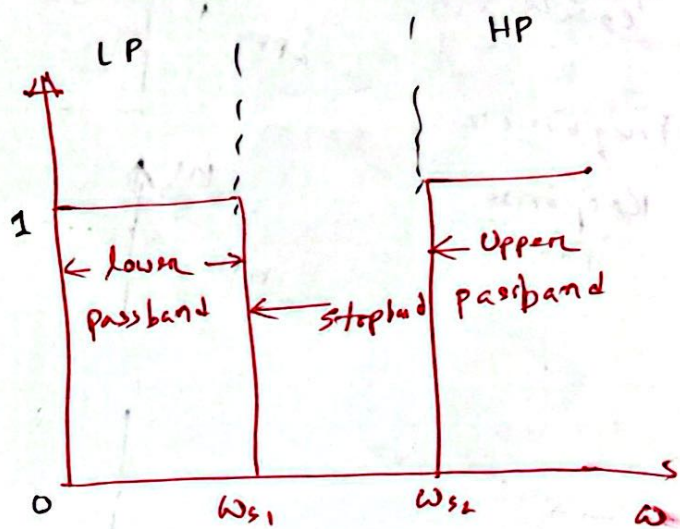



BS

Series Combination:

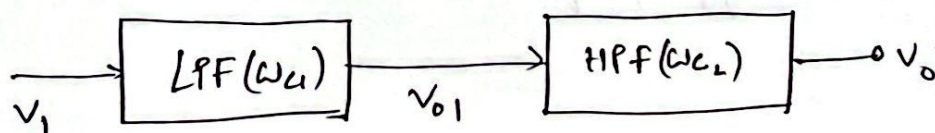

$$\omega_{c2} > \omega_{c1}$$

Frequency Response Plot

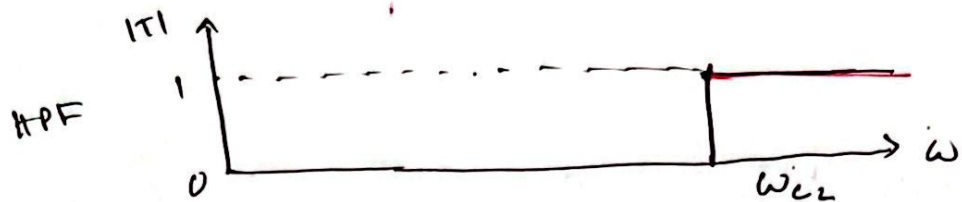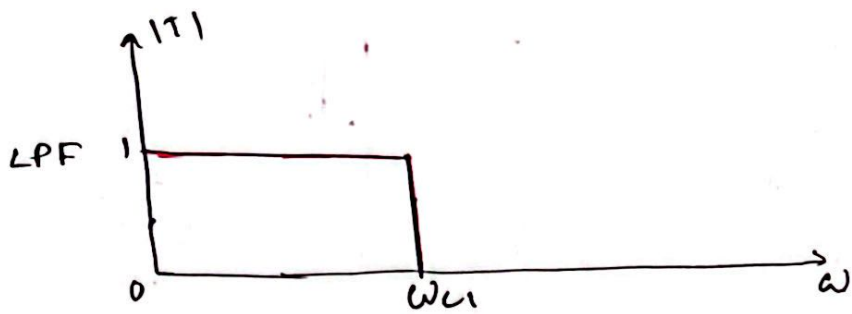


Series Combination
of HPF
LPF




$$\omega_{c2} < \omega_{c1}$$

Frequency Response Plot


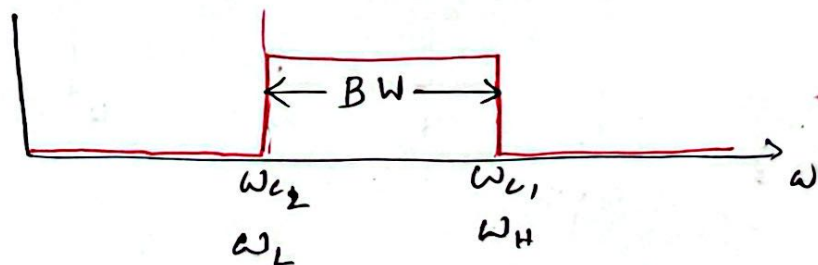


cut off freq HP < cut off freq LP.


Parallel Combination:

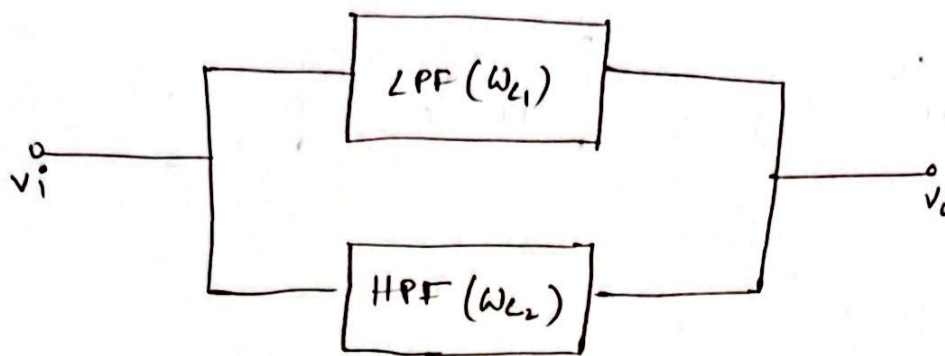



$$\omega_{L1} > \omega_{L2}$$

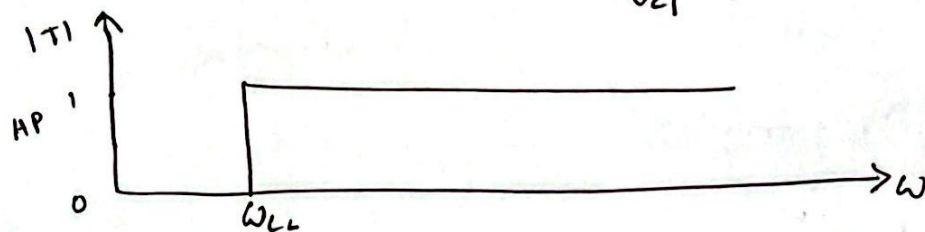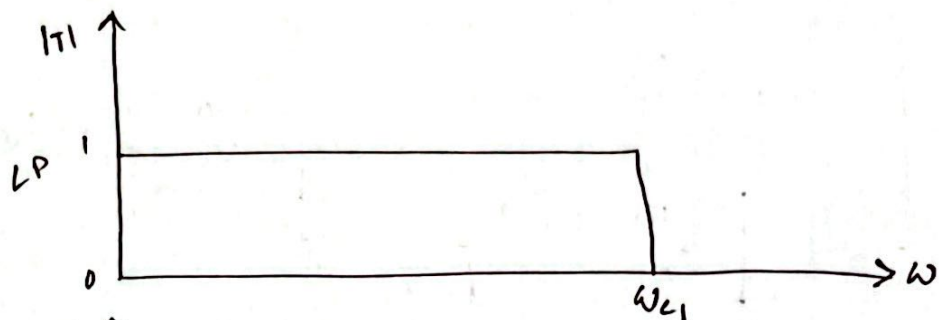


All Pass filter.

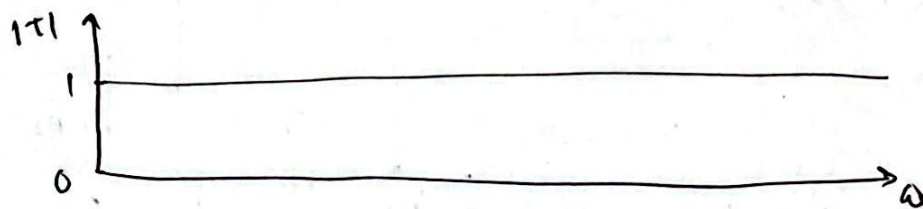


$$\omega_{L2} > \omega_{L1}$$

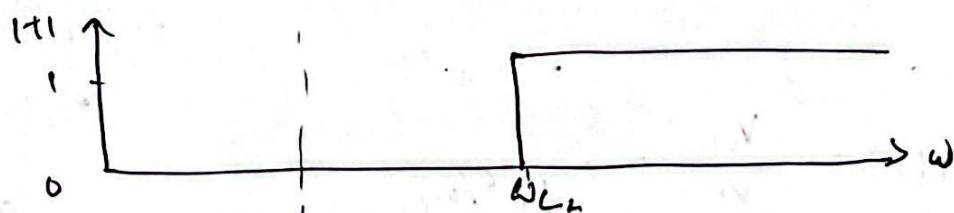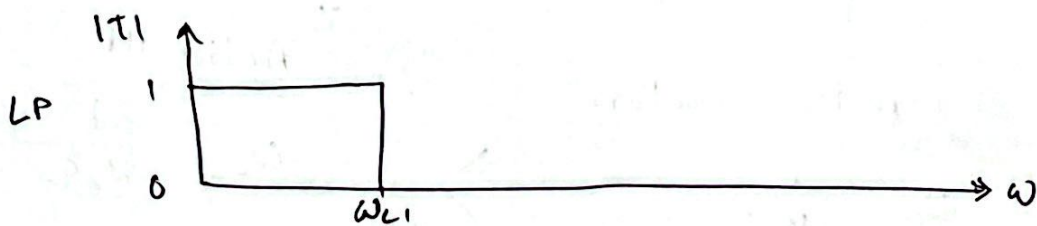

Band Stop filter.

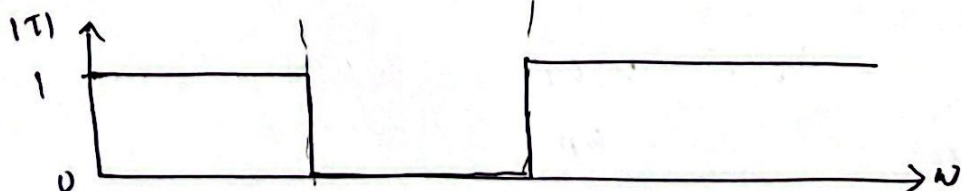


Band Pass filter:

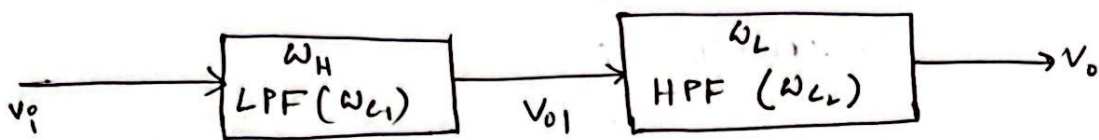


$$\omega_L < \omega_H$$

Band Stop filter:

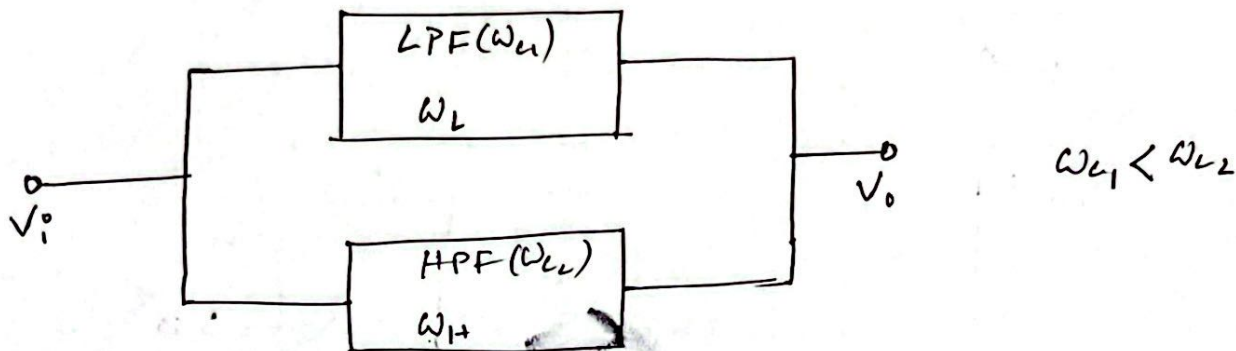

Circuit Diagram:

Band Pass:

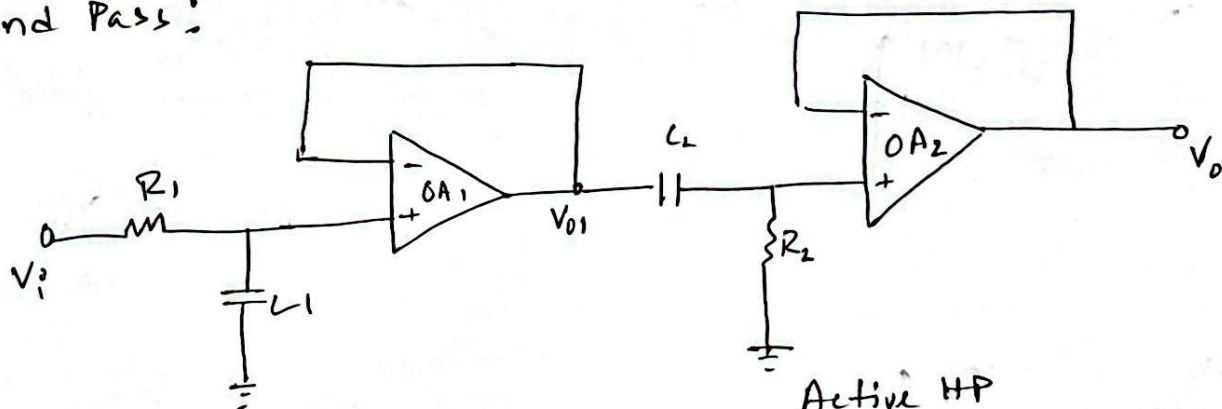

Active low Pass

$$\omega_{L1} = \frac{1}{R_1 C_1}$$

Active HP

$$\omega_{L2} = \frac{1}{R_2 C_2}$$

$$= \omega_L$$

$$T_1(s) = \frac{V_{o1}}{V_i} = \frac{1}{1 + s/\omega_{L1}}$$

$$\omega_{L1} = \frac{1}{R_1 C_1}$$

$$= \omega_H$$

$$T_2(s) = \frac{V_o}{V_{o1}} = \frac{s}{1 + s/\omega_{L2}}$$


$$\omega_{L2} = \frac{1}{R_2 C_2}$$

$$= \omega_L$$

∴ Overall transfer function,

$$\begin{aligned}
 T(s) &= \frac{V_o}{V_i} = \frac{V_o}{V_{o1}} * \frac{V_{o1}}{V_i} \\
 &= T_2(s) * T_1(s) \\
 &= \frac{1}{1 + \omega_{L1}/s} * \frac{1}{1 + s/\omega_{L1}}
 \end{aligned}$$

Max gain = 1

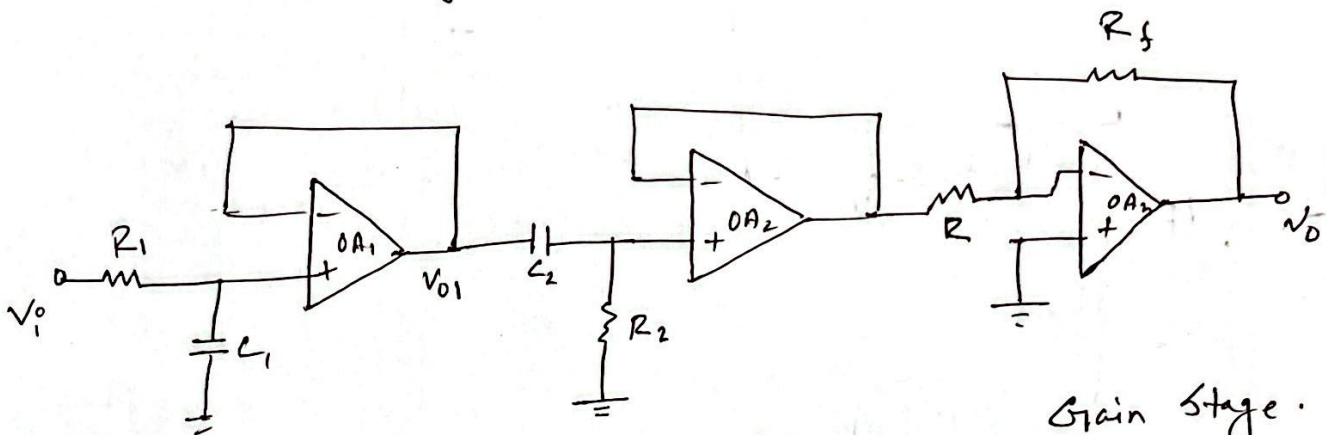

LP filter

$$T_1(s) = \frac{V_{o1}}{V_i} = \frac{1}{1 + s/\omega_{L1}}$$

HP filter

$$\begin{aligned}
 T_2(s) &= \frac{V_{o2}}{V_{o1}} \\
 &= \frac{1}{1 + \omega_{L1}/s}
 \end{aligned}$$


Gain stage.

$$\begin{aligned}
 T_3(s) &= \frac{V_o}{V_{o2}} \\
 &= -\frac{R_f}{R}
 \end{aligned}$$

∴ Overall transfer function;

$$\begin{aligned}
 T(s) &= \frac{V_o}{V_i} = \frac{V_o}{V_{o2}} * \frac{V_{o2}}{V_{o1}} * \frac{V_{o1}}{V_i} \\
 &= T_3(s) * T_2(s) * T_1(s) \\
 &= -\frac{R_f}{R} * \frac{1}{1 + \omega_{L1}/s} * \frac{1}{1 + s/\omega_{L1}}
 \end{aligned}$$

Band Stop:

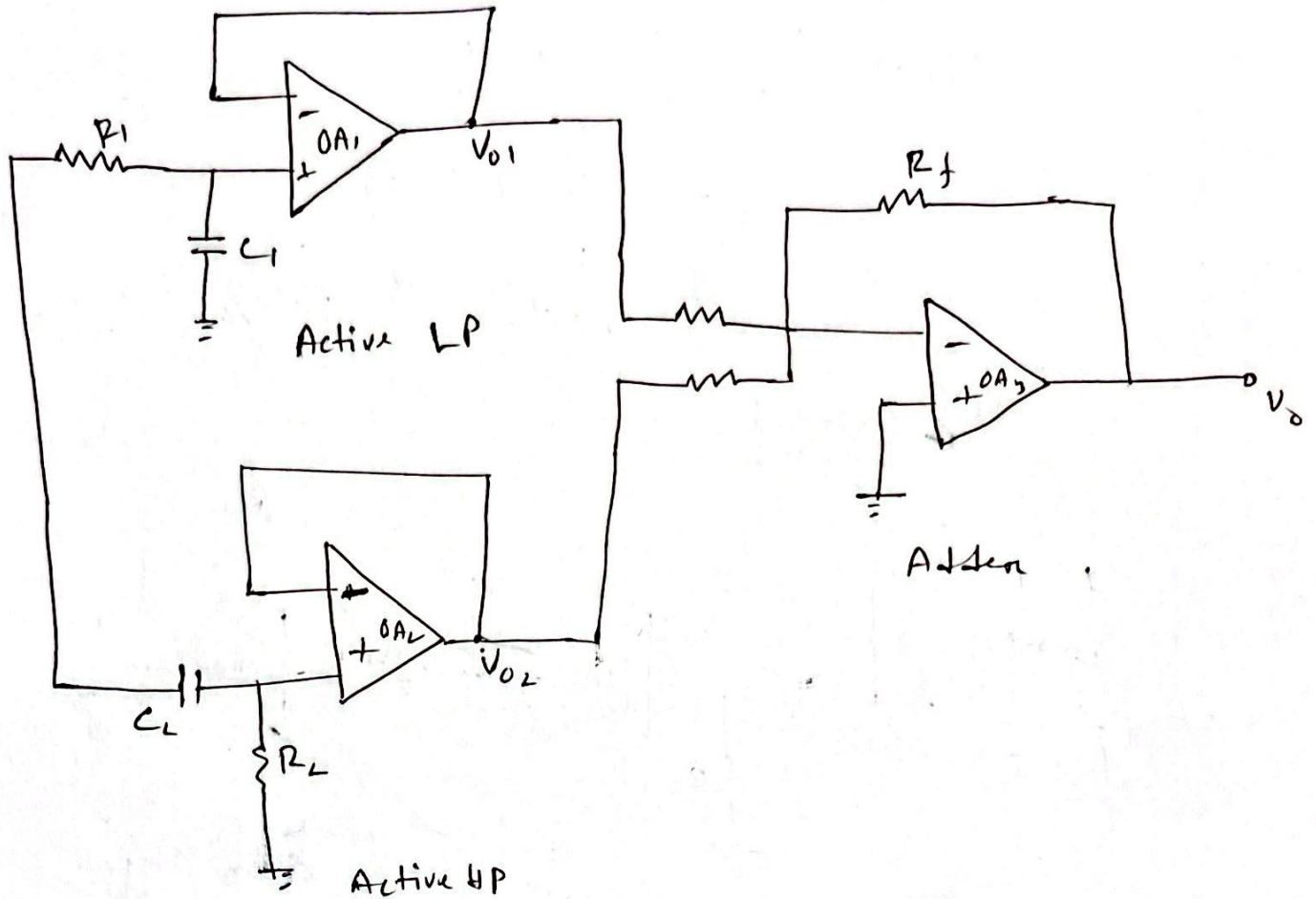

$$\omega_{L1} = \frac{1}{R_1 C_1} = \omega_L \quad \omega_{L2} > \omega_{L1} \quad \omega_{L2} = \frac{1}{R_2 C_2} = \omega_H$$

$$L.P \rightarrow T_1(s) = \frac{V_{01}}{V_i} = \frac{1}{1 + s/\omega_{L1}}$$

$$H.P \rightarrow T_2(s) = \frac{V_{02}}{V_i} = \frac{1}{1 + \omega_{L2}/s}$$

$\therefore$ Overall transfer function,

$$V_o = -\frac{R_f}{R} (V_{01} + V_{02})$$

$$\begin{aligned} T(s) = \frac{V_o}{V_i} &= -\frac{R_f}{R} \left(\frac{V_{01}}{V_i} + \frac{V_{02}}{V_i} \right) \\ &= -\frac{R_f}{R} (T_1(s) + T_2(s)) \\ &= -\frac{R_f}{R} \left(\frac{1}{1 + s/\omega_{L1}} + \frac{1}{1 + \omega_{L2}/s} \right) \end{aligned}$$