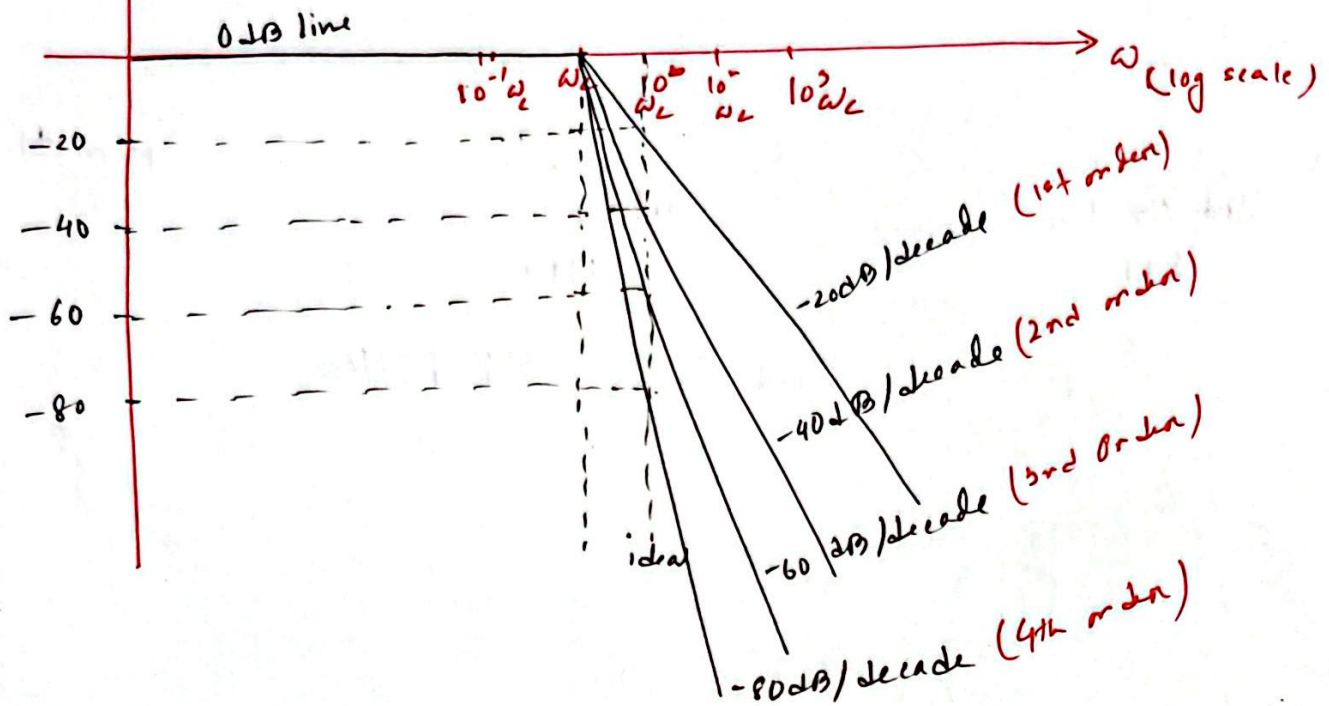


Higher Order Filters:





Merits:

- ① Filter characteristics closer to ideal filter
- ② more effective in filtering out unwanted signals, resulting in more accurate and less noisy output.

Demerits

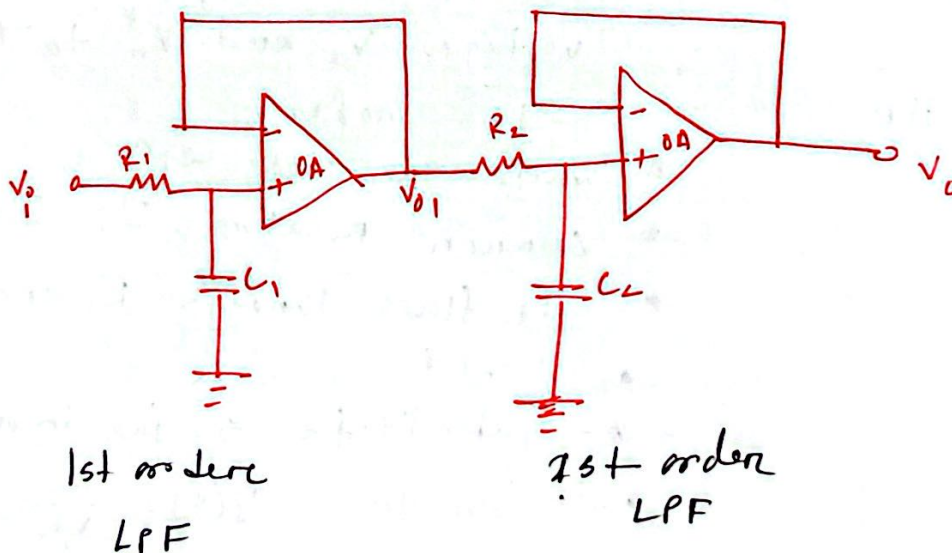
- ① More circuit components
- ② Consumes more power
- ③ Occupies more space.
- ④ Cost more.



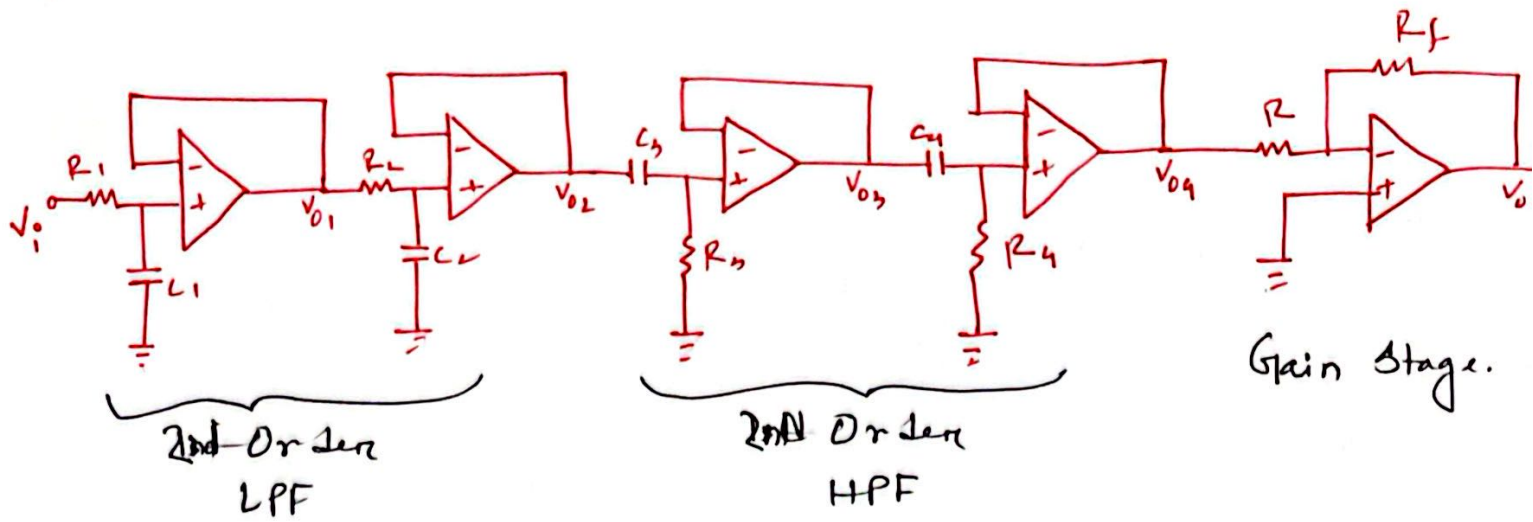


2nd Order BP Filter.

Sallen and Key filters:

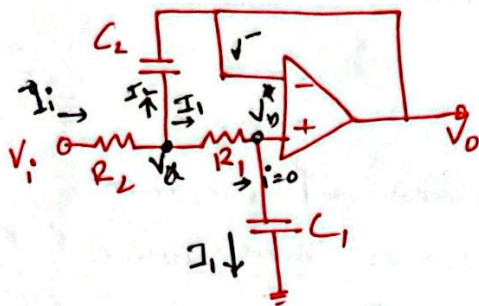

2nd Order LP

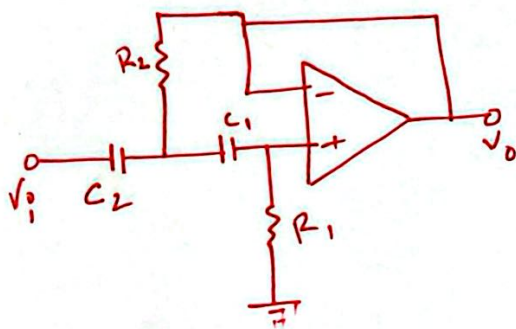

2nd Order HP

Merits!

- Use only one op-amp to construct a 2nd order filter.
- Less circuit component
- Consumes less power
- Consumes less space
- Cost less.

- * Identify and assign node voltages V_a and V_b to the two nodes.
- * Write the node eqn
- * Current relation, $I_i = I_1 + I_2$
- * I_1 flows through R_1 and C_1
- * $V^+ = V^- = V_o$
- * substitute $s = j\omega$ in node eqn
- * Solve for, $T(s) = \frac{V_o}{V_i}$

2nd Order LP filter:

$$T(s) = \frac{V_o}{V_i} = \frac{\omega_o^2}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$

$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \rightarrow \text{cut off freq}$$

$$\frac{\omega_o}{Q} = \frac{1}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$Q = \frac{1}{\sqrt{2}} \quad \text{For } \omega_o \text{ to be the cut off freq.}$$


2nd Order HP filter:

$$T(s) = \frac{V_o}{V_i} = \frac{s^2}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2}$$

$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{\omega_o}{Q} = \frac{1}{R_1} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$


$$Q = \frac{1}{\sqrt{2}}$$

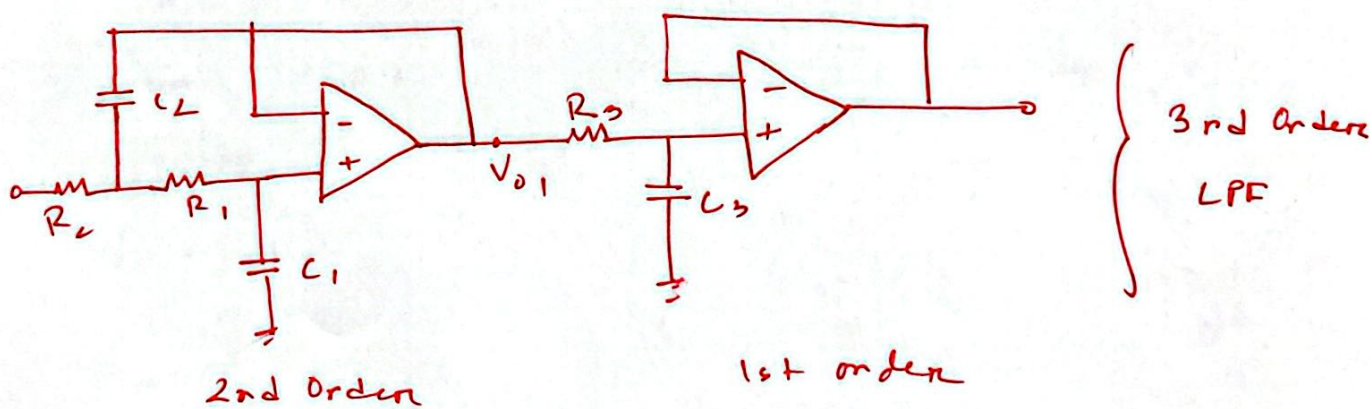

3rd Order LPF $\rightarrow$ 2nd Order LPF + 1st Order LPF
 4th " " $\rightarrow$ 2nd Order LPF + 2nd Order LPF
 5th " " $\rightarrow$ 2 2nd Order + 1 1st order LPF.

3rd Order BSF

3rd Order LPE

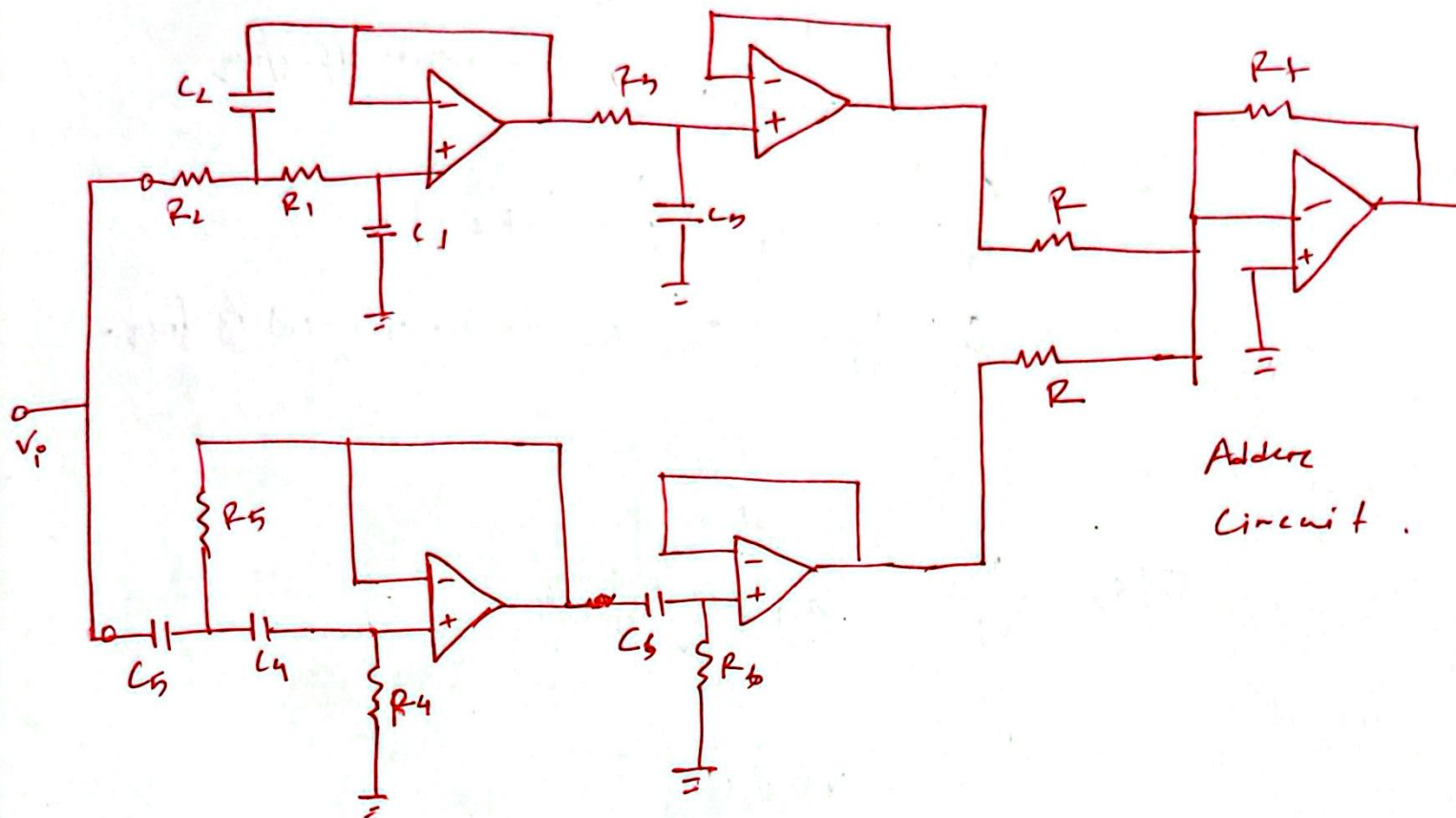

3rd Order HPF

Adder
Circuit .